

FUNDAMENTALS OF ELECTRICAL AND ELECTRONICS ENGINEERING

(ECE-1002)



Dr.Jayendra kumar
(70077)

Taran(19BCE7346)

● LIST OF EXPERIMENTS

Content Outlines		
Weeks	Topics	Task/Reading
1	Experiment #1: Ohm's Law & Series and parallel circuits	Experiment #1
2	Experiment #2: Kirchoff's current law	Experiment #2
3	Experiment #3: kirchoff's voltage law	Experiment #3
	Experiment #4: Thevenin's and Norton's theorem and Maximum power transfer theorem	Experiment #4
4	Experiment #5: Superposition Theorem	Experiment #5
5	Experiment #6: verification of diode	Experiment #6
6	Experiment #7: design of half rectifier	Experiment #7
7	Experiment #8: design of Bridge rectifier with and without capacitor	Experiment #8
9	Experiment #9: BJT Characteristic and Biasing Circuits	Experiment #9

EXPERIMENT NO.1

TITLE : verification of ohm's law (simulation)

OBJECTIVE :

- *To verify Ohm's law ($V=IR$) where current through a resistor is proportional to the voltage across it.*
- *To verify that in a series circuit;*
 - *The total resistance is equal to the sum of the individual resistors.*
 - *The voltage drops across the resistors equals to the applied voltage.*
 - *The value of the current is the same in all parts of the circuit.*
- *To verify that in parallel circuits;*
 - *The equivalent resistance is the reciprocal of the sum of reciprocals of the individual resistors.*
 - *The branch current in parallel equal to the supply current.*
 - *The voltage drop across each resistor in parallel is the same.*
 - *To verify by measurement and calculation for two different networks: the total current and the branch values, the voltage drop across various parts of the networks and the method for determining the equivalent resistance of such networks.*
- *Equipments :*
 - *Instruments*
 - *DC power supply*
 - *Two digital multimeters.*
 - *Resistors ; $1.0k\Omega$, $1.5k\Omega$, $6.8k\Omega$*

EQUIPMENT : computer and ni multisim software

ECE LAB REPORT

CIRCUIT DIAGRAM :

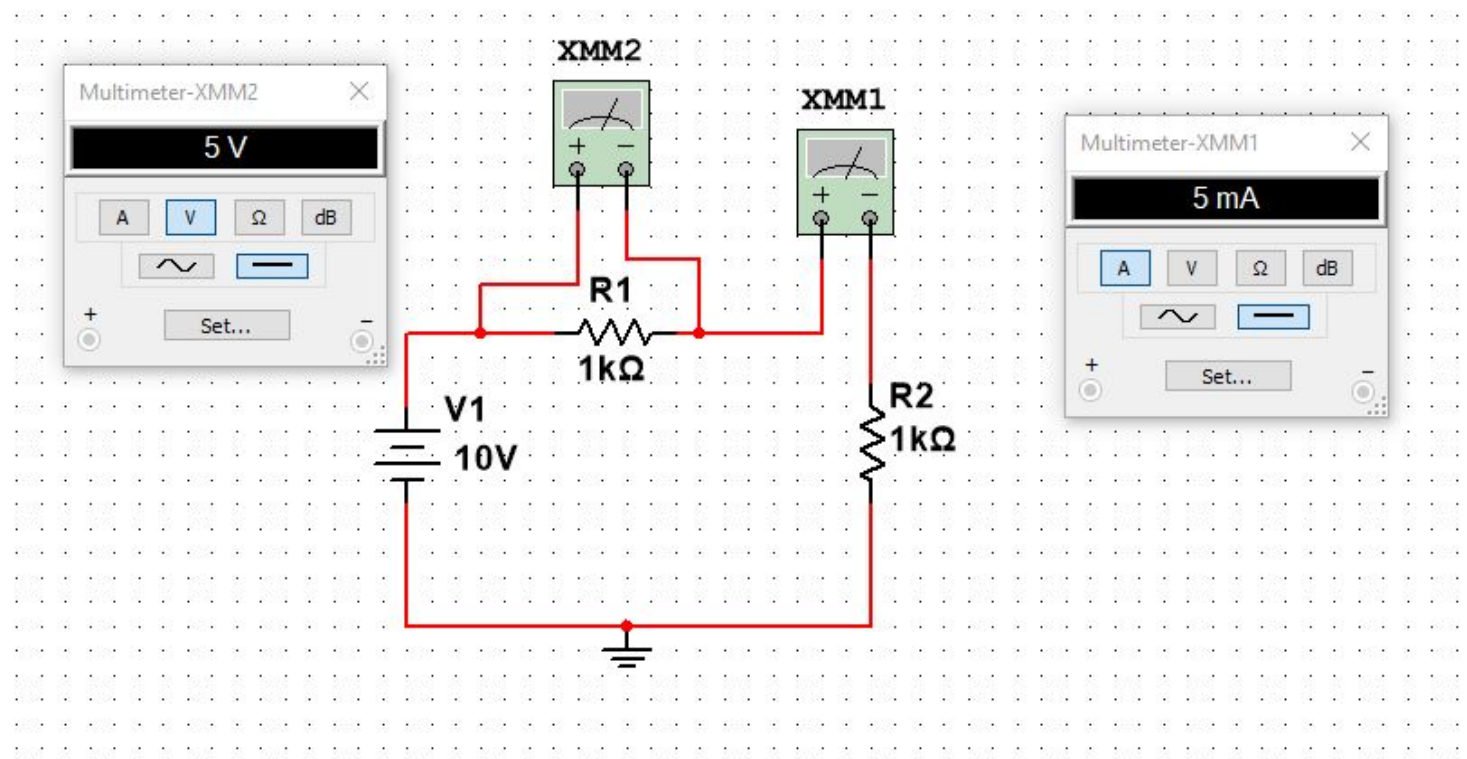


FIG 1 DC CIRCUIT

ECE LAB REPORT
EXPERIMENT NO. 2

TITLE: Kirchhoff's Current Law

Objective:

- a) To verify Kirchhoff's current laws.

Equipment:

Instruments

DC power supply

Three digital multimeters.

Components

Resistors ; 300Ω (2), 330Ω , $1.8\text{ k}\Omega$, $2.7\text{ k}\Omega$, $3.0\text{ k}\Omega$


Procedures:

Part A : Kirchhoff's Current Law:

1. Measure the branch currents entering node A by placing ammeter as shown in *FIG*
2. Record the magnitude and the direction of the current as indicated by each ammeter in *Table*

CIRCUIT DIAGRAM :

ECE LAB REPORT

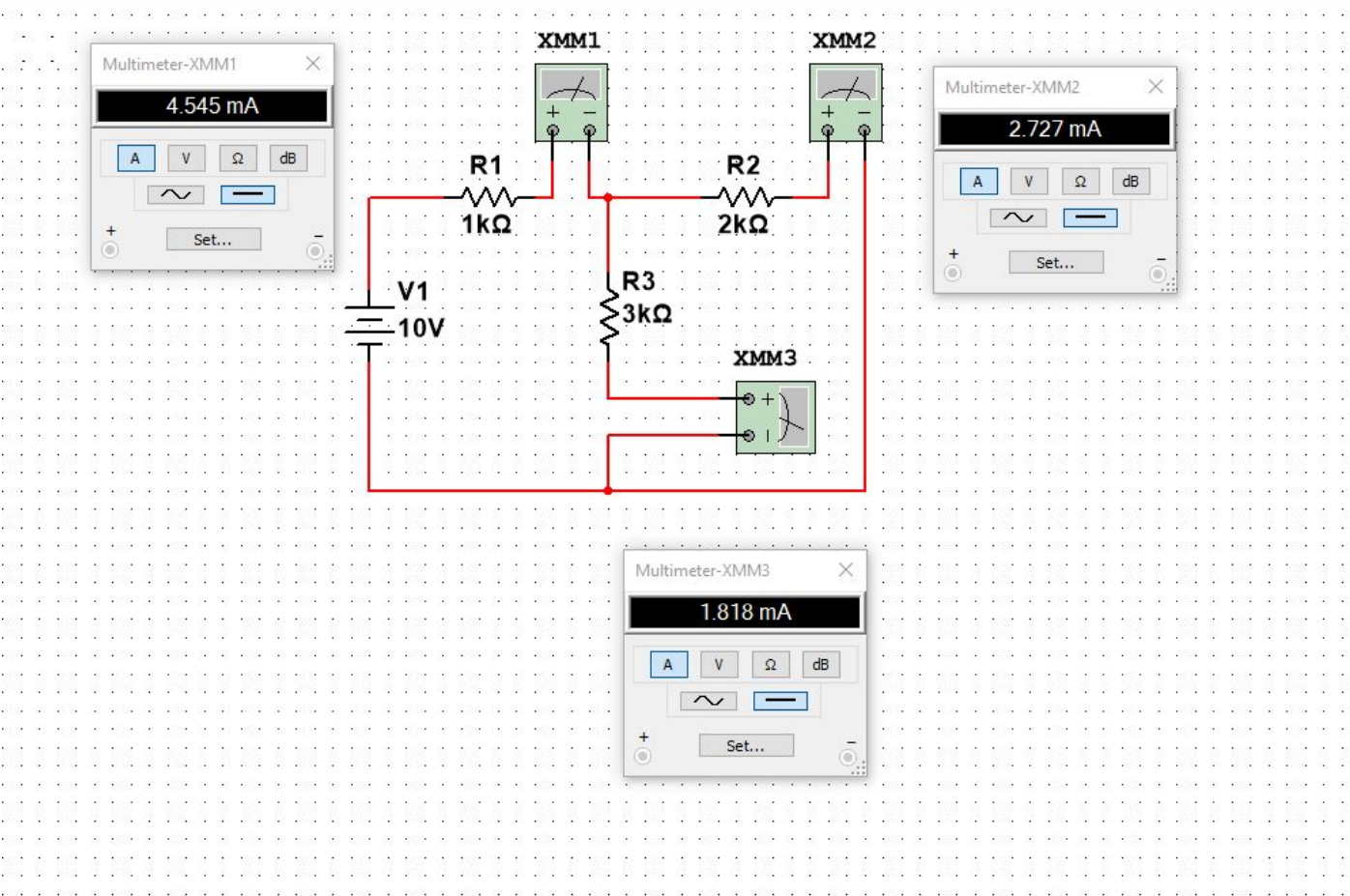

EXPERIMENT NO.3

Objective:

- b) To verify Kirchhoff's voltage laws.

Equipment:

Instruments

DC power supply

Three digital multimeters.

Components

Resistors ; 300Ω (2), 330Ω , $1.8\text{ k}\Omega$, $2.7\text{ k}\Omega$, $3.0\text{ k}\Omega$


Part A: Kirchhoff's Voltage Law:

- Measure the resistance of each resistor. Set the supply voltage to 10V. Record the measured values in *Table*
- Construct the circuit shown in
- Commence at point A and measure the potential difference between each successive pair of lettered terminals for Mesh 1. i. e. A-B, B-C, C-D and D-A.

(Note: DMM's probes have to be placed consistently.)

- Record down the measured values in *Table*
- Measure the potential difference for the points AC, CE and EA. Verify Kirchhoff's voltage law using the displayed values. (Note that V_{CA} is actually $V_C - V_A$). What can be deduced from this condition? Record the measured values in *Table*

CIRCUIT DIAGRAM :

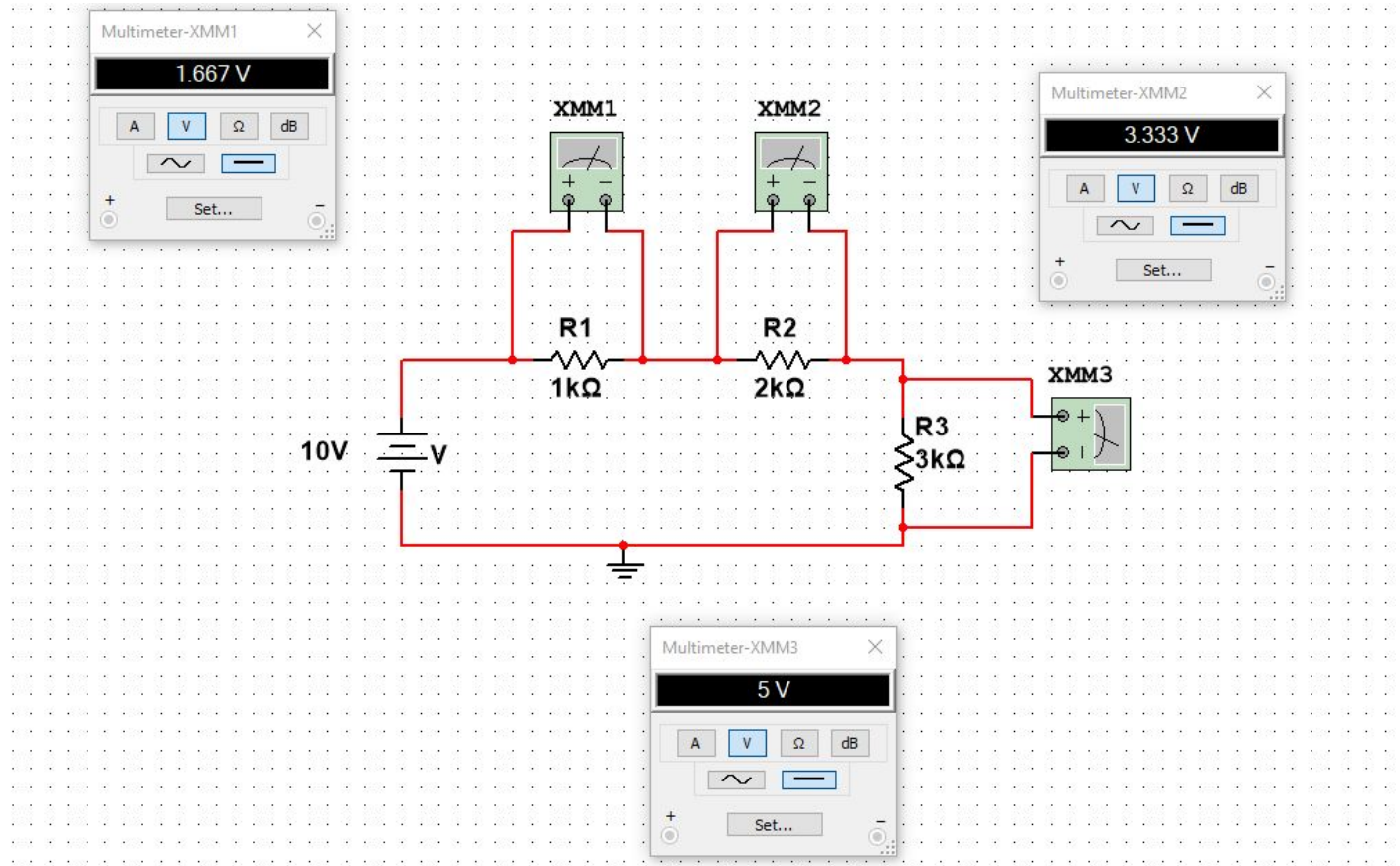

ECE LAB REPORT**EXPERIMENT NO. : 4****Title : Thevenin's & Norton's Theorem and Maximum Power Transfer Theorem****Objectives:**

- a) To applied Thevenin's and Norton's theorems in finding the current flowing in a particular resistor (variable load) in a particular network.
- b) To verify the theorems by comparing the simulated values to those obtained by measurement.
- c) To verify the maximum power transfer theorem.

Equipment:Instruments


DC power supply

Digital multimeters

ComponentsResistors 1.8k Ω ; 3.6k Ω ; 820 Ω ; 100 Ω (2); 180 Ω

Rheostat (2)

Diagram :

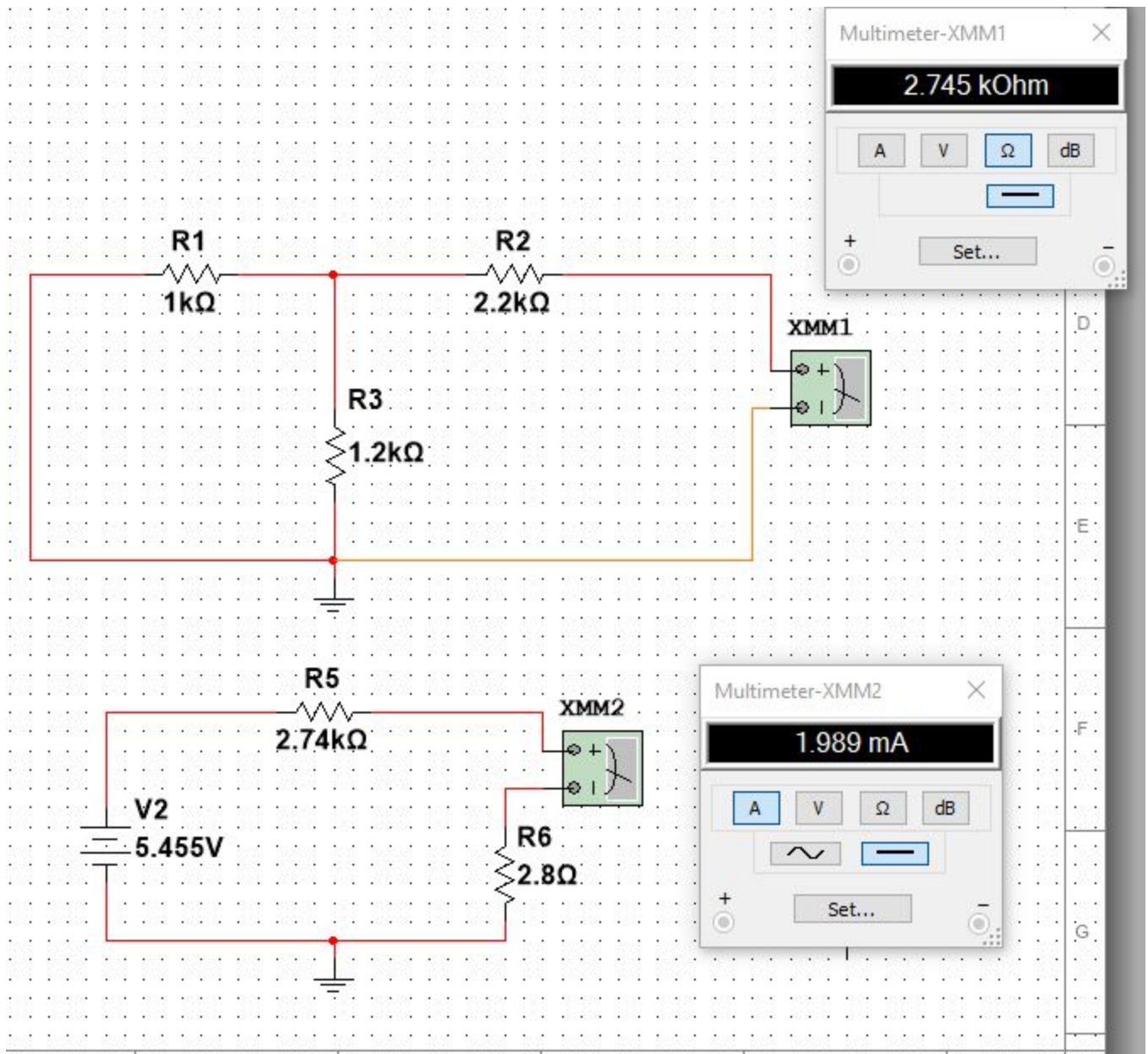ECE LAB REPORT

ECE LAB REPORT**EXPERIMENT NO. : 5****TITLE : Superposition Theorem****Objective:**

To verify experimentally the Superposition theorem which is an analytical technique of determining currents in a circuit with more than one EMF source.

Equipment:Instruments

Two DC power supplies of suitable voltage and current ratings.

Three DC voltmeters (0-5 V).

One multimeter.

Trainer board

Components

Three potentiometers (10 k Ω)

Procedures:

1. Set up the network (circuit) as in *Fig. 3.1*.
2. Keep both sources active in the circuit by keeping the poles of SPDT s in proper position.
3. Apply 5 volts from E_1 and 10 V from E_2 .
4. Set the rheostats R_1 , R_2 , R_3 at such value so that none of the ammeter readings I_1 , I_2 , I_3 exceeds the power supplies (E_1 and E_2 current ratings and the rheostat current) ratings.
5. Measure the current I_2 and record it in *Table 1*.
6. Render E_2 inactive.
7. Measure the current I_2' in the branch R_2 and record it in *Table 1*.
8. Render E_1 inactive.
9. Measure the current I_2'' in the branch R_2 and record it in *Table 1*.
10. Verify if $I_2 = I_2' + I_2''$ which would validate the superposition theorem for this particular circuit.
11. Repeat steps 4 to 10 by changing R_1 , R_2 , and R_3 and take a few more sets of readings.
12. Find theoretically the current I_2 with reference to *Fig. 3.1* by applying the superposition theorem considering $E_1 = 15$ volts, $E_2 = 20$ volts and R_1 , R_2 , R_3 at their measured values recorded in *Table*

CIRCUIT DIAGRAM :


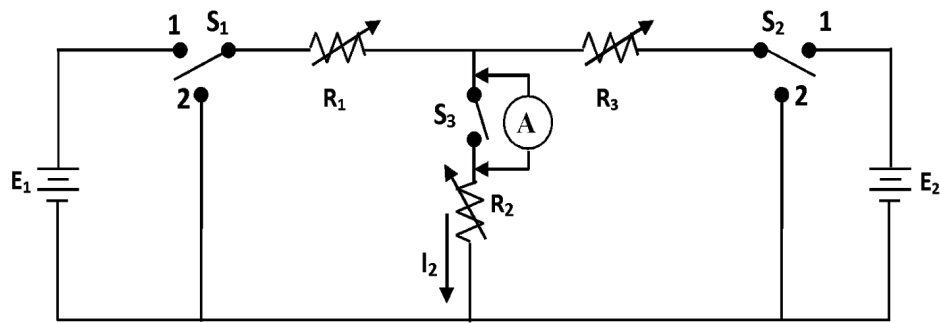


Fig. 3.1

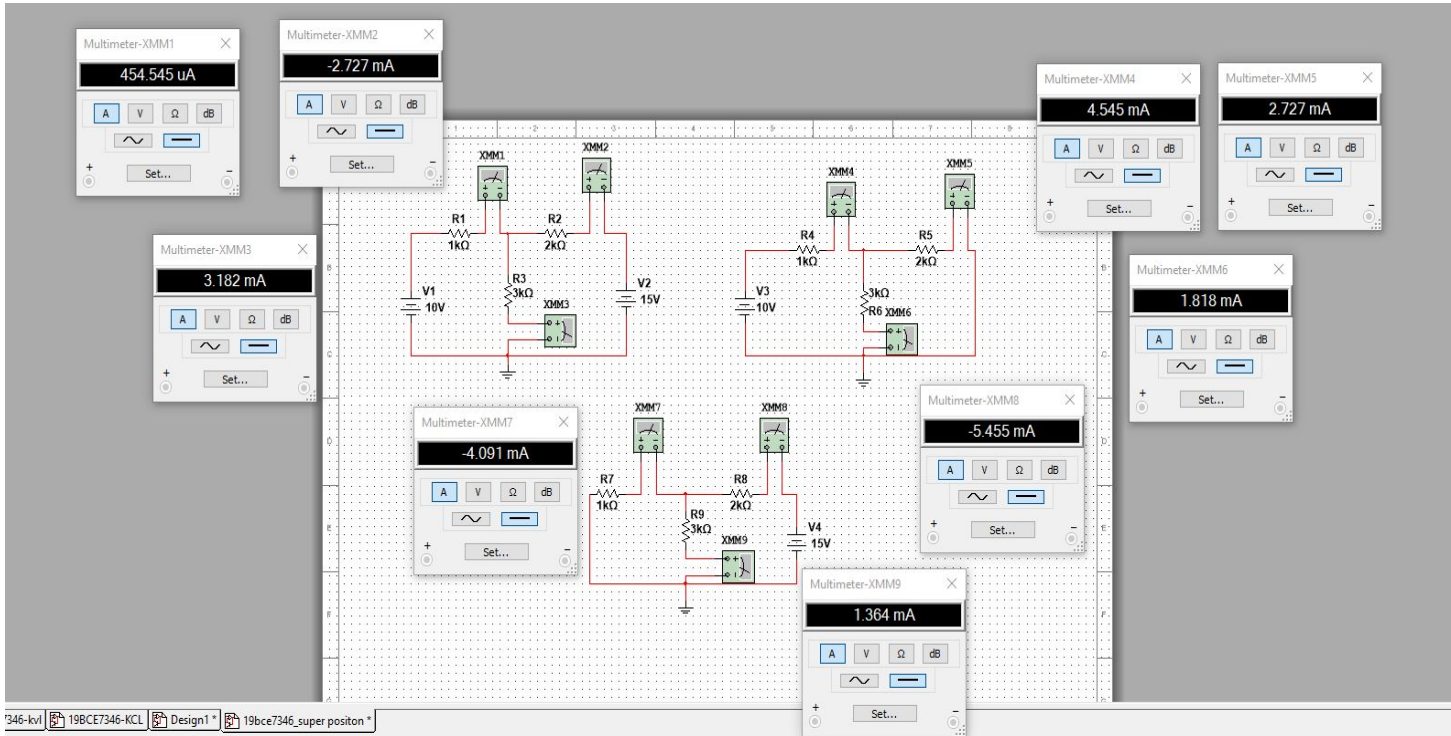

EXPERIMENT NO. : 6

Title : Diode Characteristic and Application

Objectives:

- a. To study the characteristics of a silicon (Si) diode and a germanium (Ge) diode.
- b. To calculate and draw the DC output voltages of half-wave



Equipment:

Instruments

DC power supply
2 Digital Multimeters (DMM)
Function Generator
Oscilloscope

Components


Silicon Diode (D1N4002), Germanium Diode (1N34A)
Resistors: 1k Ω
Resistors: 2.2k Ω , 3.3k Ω

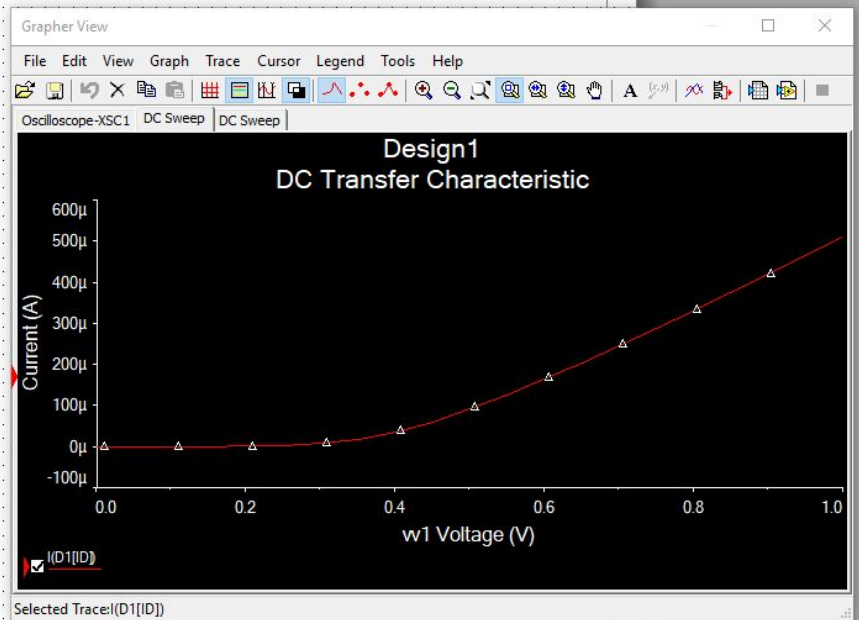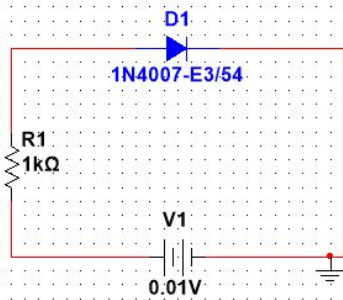Circuit diagram :

EXPERIMENT NO.7

Title : design of half rectifier

Circuit diagram :

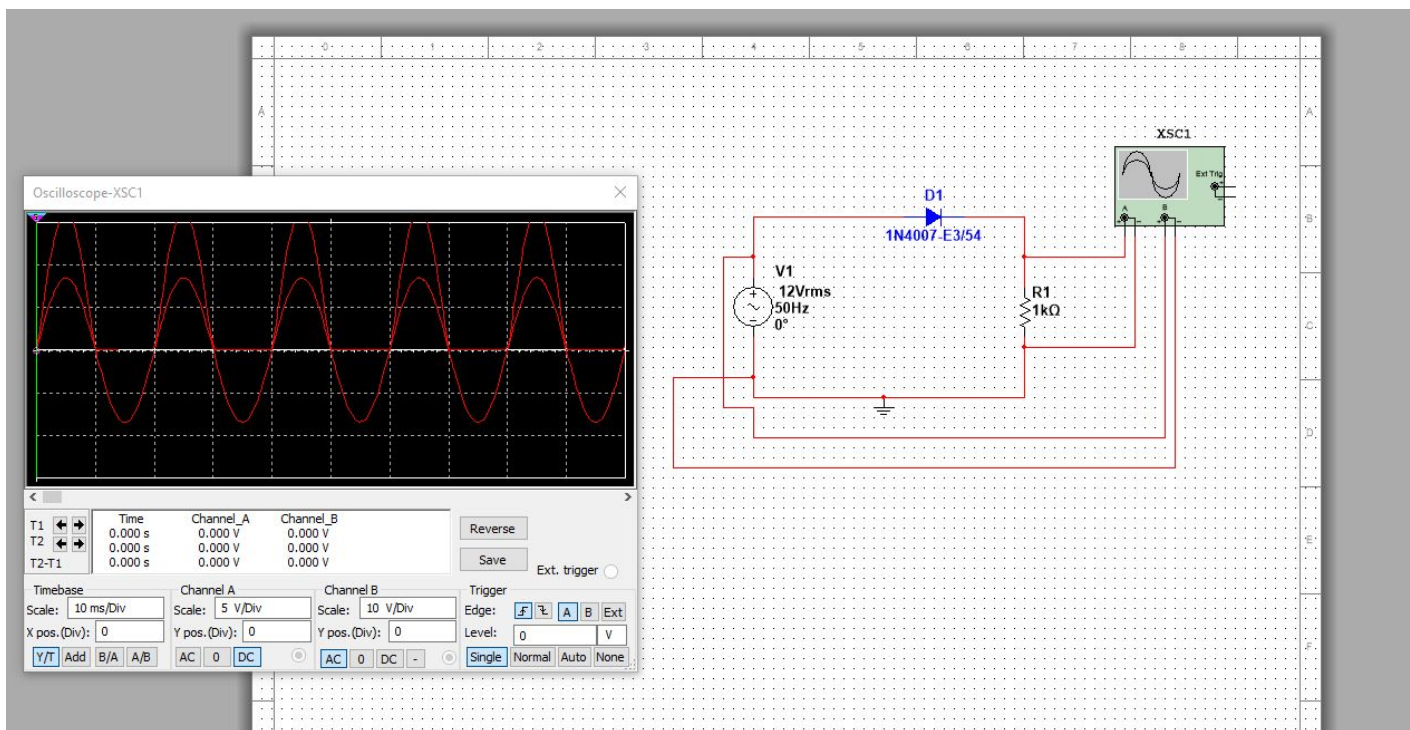

ECE LAB REPORT

EXPERIMENT NO.8

TITLE : design of bridge rectifier with and without capacitor

CIRCUIT DIAGRAM :

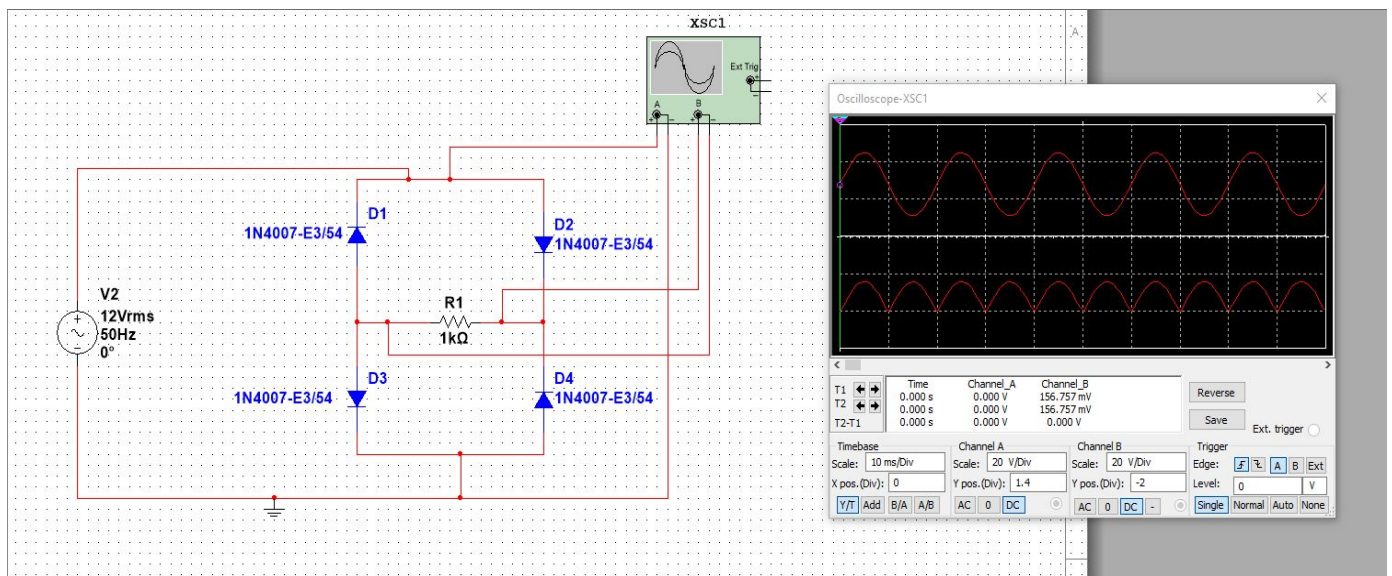


Fig : Bridge rectifier with out capacitor

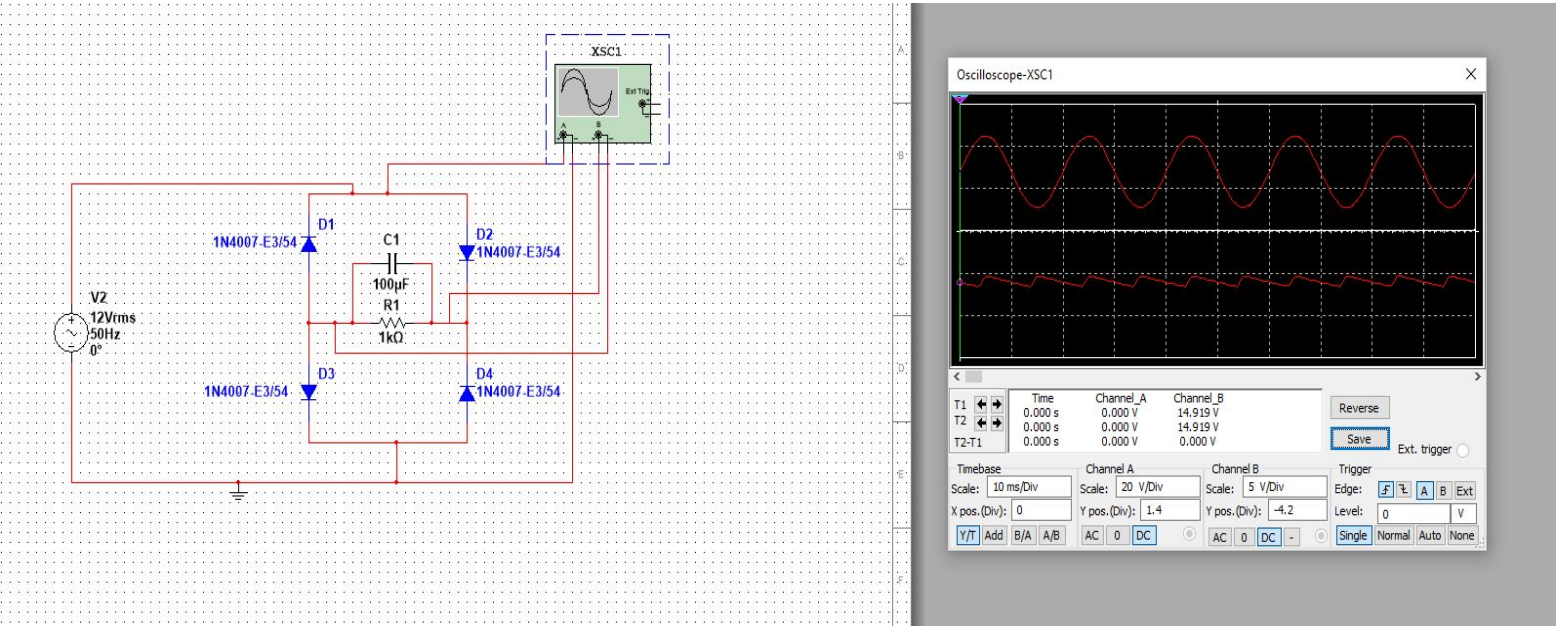


Fig : Bridge with capacitor

ECE LAB REPORT

EXPERIMENT NO. 9

TITLE : BJT Characteristics & Biasing Circuits

Objectives:

- a) To provide the characteristics of a transistor using experimental methods.
- b) To determine the quiescent operating conditions of a voltage-divider-bias BJT configurations.

Equipment:

Instruments

1 DC Power Supply

3 Digital Multimeter (DMM)

Components

Resistors: $680\ \Omega$, $6.8\ \text{k}\Omega$, $1\ \text{k}\Omega$, $3\ \text{k}\Omega$, $22\ \text{k}\Omega$, $330\ \text{k}\Omega$, $10\ \text{k}\Omega$ potentiometer, $1\text{M}\Omega$ potentiometer

Transistors: 2N3904

Circuit diagram :

